

# Fault Detection of VLSI/SoC/IC Testing

---

Dr. Katherine Shu-Min Li  
EDA&T Lab.

Dept. Computer Science and Engineering  
National Sun Yat-Sen University  
Kaohsiung, TAIWAN



Thanks to Prof. Sying-Jyan Wang, [sjwang@cs.nchu.edu.tw](mailto:sjwang@cs.nchu.edu.tw)

# Review:

## How To Do Test: **FIVE** Approaches

---

- ❑ **Fault Modeling**
  - Identify **target faults**
  - Limit the **scope of test generation**
  - Make analysis possible
- ❑ **Test Generation**
  - Automatic or Manual
- ❑ **Fault Simulation**
  - Assess completeness of tests (test patterns), fault/test coverage
- ❑ **Testability Analysis**
  - Analyze a circuit for potential problems on test generation
- ❑ **Design For Testability**
  - Input for **Controllability**; Output for **Observability**
  - Design a circuit for guaranteed test generation
  - Introduce both area overhead and performance degradation



# Review:

## Fault Modeling

---

### □ Fault Models

- Stuck-At Faults
- Bridging Faults
- Transistor Stuck-On/Open Faults
- IDDQ Faults
- Functional Faults
- Memory Faults
- PLA Faults
- Delay Faults & State Transition Faults



# Fault Detection

---

- ❑ Why **Logical** Fault Modeling
- ❑ Fault Detection
- ❑ Sensitization
- ❑ Detectability
- ❑ Undetectable Faults
- ❑ Test Set
- ❑ Test Generation Flow
- ❑ Fault Equivalence
  - Equivalence Fault Collapsing



# Why **Logical** Fault Modeling

---

- ❑ Fault analysis on logic rather than physical defect problem
  - **Complexity is reduced**
- ❑ **Technology independent**
  - Same **fault model** is applicable to many technologies
  - **Testing and diagnosis methods** remain valid despite changes in technology
- ❑ **Tests/Test Inputs** derived may be used for physical faults
  - Physical faults/defects effect on circuit behavior is not completely understood or too complex to be analyzed
- ❑ **Stuck-at fault**: The **most popular logical fault model**



# Fault Detection

---

- ☐ **Why Logical Fault Modeling**
- ☐ **Fault Detection**
- ☐ **Sensitization**
- ☐ **Detectability**
- ☐ **Undetectable Faults**
- ☐ **Test Set**
- ☐ **Test Generation Flow**
- ☐ **Fault Equivalence**
  - **Equivalence Fault Collapsing**




# Fault Detection

□ A **test(vector)  $t$**  detects a fault  **$f$**  if and only if

■  $t$  detects  $f \Leftrightarrow \mathbf{z}_f(t) \neq \mathbf{z}(t)$

□ Example

 ■  $t=(100)$  detects  $f$  because  $\mathbf{z}_1(\mathbf{100})=\mathbf{0}$  and  $\mathbf{z}_{1f}(\mathbf{100})=\mathbf{1}$



$$\mathbf{Z}_1 = \mathbf{X}_1\mathbf{X}_2$$

$$\mathbf{Z}_2 = \mathbf{X}_2\mathbf{X}_3$$

$$\mathbf{Z}_{1f} = \mathbf{X}_1$$

$$\mathbf{Z}_{2f} = \mathbf{X}_2\mathbf{X}_3$$

Summary:  $X2 = X2\_stem + \mathbf{X2\_up\_fanout(sa1, s-a-1)} + \mathbf{X2\_down\_fanout}$



# Fault Detection


---

- ☐ **Why Logical Fault Modeling**
- ☐ **Fault Detection**
- ☐ **Sensitization**
- ☐ **Detectability**
- ☐ **Undetectable Faults**
- ☐ **Test Set**
- ☐ **Test Generation Flow**
- ☐ **Fault Equivalence**
  - **Equivalence Fault Collapsing**





# Sensitization (1/2)

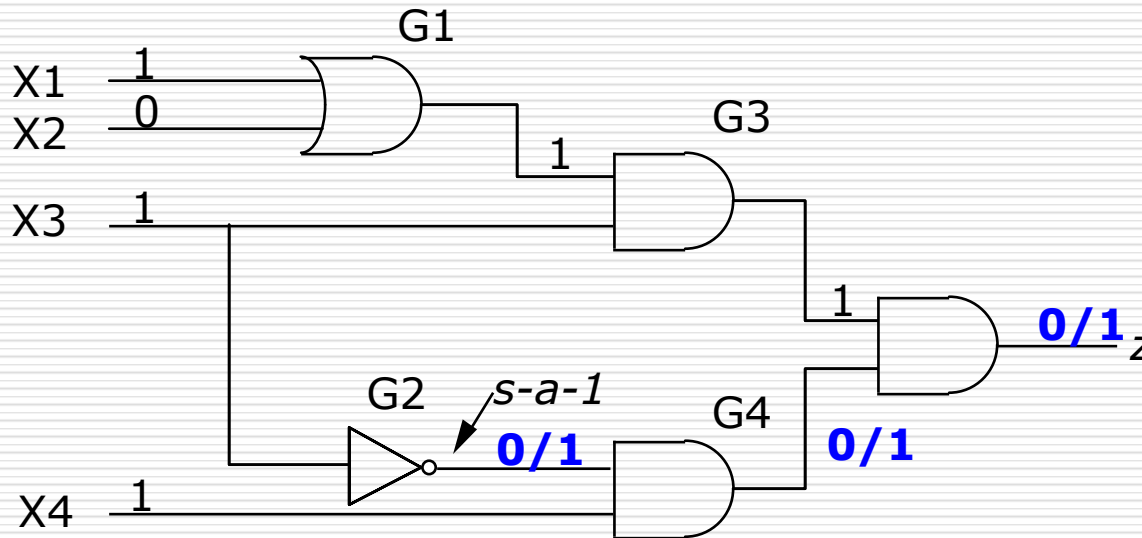

$$Z(1011) = 0$$

$$Z_f(1011) = 1$$

□ 1011 detects the fault  $f$  (**G2 stuck-at 1**)

□  $v/v_f$

■  $v$  = signal **v**alue in the **fault free** circuit

■  $v_f$  = signal **v**alue in the **faulty** circuit



# Sensitization (2/2)

- A test/test input  $t$  detects a fault  $f$ 
  - **Step 1. FA: Activate  $f$**  (or **generate a fault effect**)
    - by creating different  $v$  and  $v_f$  values at the site of the target fault  $\Rightarrow \mathbf{v/v_f}$
    - $\Rightarrow$ Test Input $\Rightarrow$ Controllability
  - **Step 2. FP: Propagate** the error to a **primary output  $w$** 
    - by making all the lines along **at least one path between the fault site and  $w$**
    - $w$  have different  $v$  and  $v_f$  values
    - $\Rightarrow$ Observability
- A line whose value in the test/test input changes in the presence of the fault  $f$  is said to be **sensitized to the fault  $f$  by the test/test input**
- A path composed of sensitized lines is called a **sensitized path**



# Fault Detection

---

- ❑ **Why Logical Fault Modeling**
- ❑ **Fault Detection**
- ❑ **Sensitization**
- ❑ **Detectability**
- ❑ **Undetectable Faults**
- ❑ **Test Set**
- ❑ **Test Generation Flow**
- ❑ **Fault Equivalence**
  - **Equivalence Fault Collapsing**



# Detectability

---

- A fault  $f$  is said to be **detectable** if there exists **a test/test input  $t$  that detects  $f$** ; otherwise,  $f$  is an undetectable fault
- For an **undetectable** fault  $f$ 
  - **No test** can simultaneously **activate  $f$**  and **create a sensitized path** to a **primary output**
  - **Step 1 Fault Activation** and **Step 2 Fault Propagation (sensitization)** need to be **satisfied at the same time**



# Fault Detection

---

- ☐ **Why Logical Fault Modeling**
- ☐ **Fault Detection**
- ☐ **Sensitization**
- ☐ **Detectability**
- ☐ **Undetectable Faults**
- ☐ **Test Set**
- ☐ **Test Generation Flow**
- ☐ **Fault Equivalence**
  - ☒ **Equivalence Fault Collapsing**




# Undetectable Faults (1/3)

---

- A fault  $f$  is said to be detectable if there exists a test  $t$  that detects  $f$ ; otherwise,  $f$  is an undetectable fault
- For an **undetectable** fault  $f$   
$$z_f(x) = z(x) \quad \text{for all } x$$
  - No test can simultaneously activate  $f$  and create a sensitized path to a primary output




# Undetectable Faults (2/3)

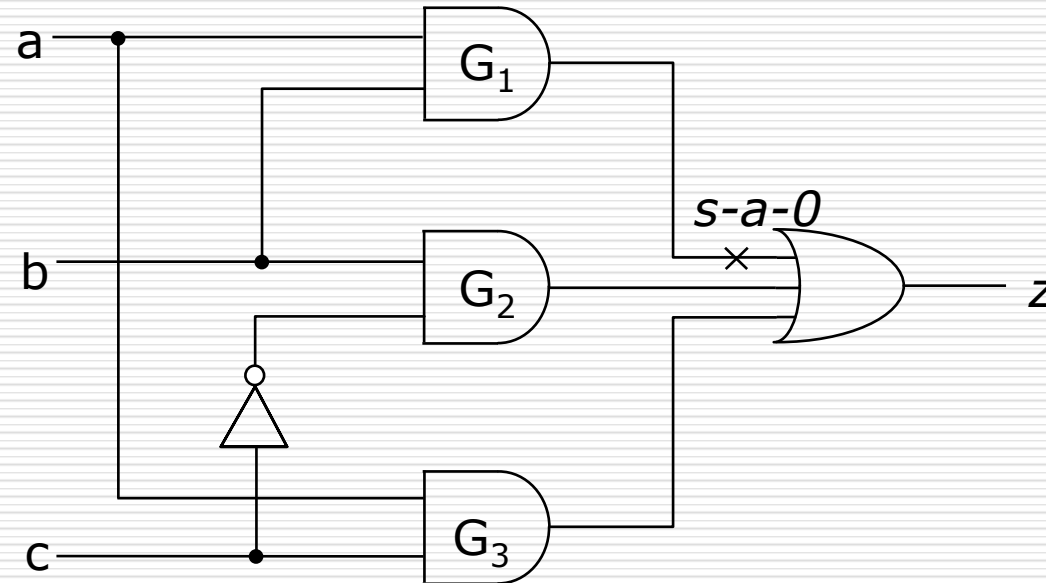

- ❑  $G_1$  output stuck-at-0  $\Rightarrow \mathbf{1/0}$
- ❑  $Z_f = \text{OR}(G_1, G_2, G_3) = 1$ ,  $Z = \text{OR}(G_1, G_2, G_3)$
- ❑  $\mathbf{G_2=0}$  and  $\mathbf{G_3=0}$  and  $\mathbf{G_1=ab=1}$
- ❑  $\mathbf{G_1=ab=1} \Rightarrow \mathbf{a=1}$  and  $\mathbf{b=1}$
- ❑  ~~$\mathbf{G_2=b \cdot \text{inv}(c)=0} \Rightarrow \mathbf{c=1}$  and  $\mathbf{G_3=ac=0} \Rightarrow \mathbf{c=0}$~~
- ❑ Thus, **conflict at  $c \Rightarrow$  No test vector available**



# Undetectable Faults (3/3)

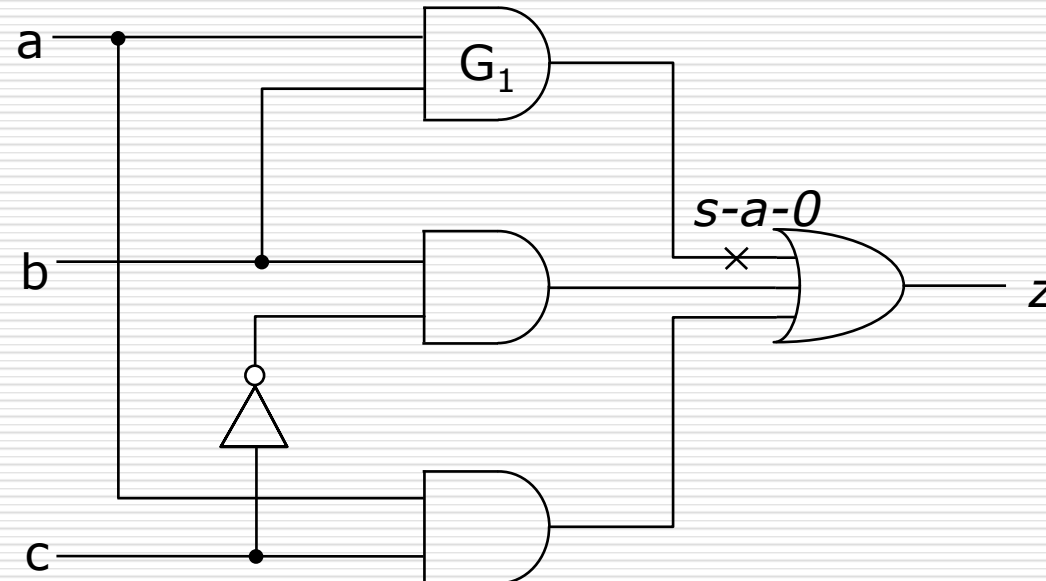

- $G_1$  output stuck-at-0 fault is undetectable
  - Undetectable faults **do not change the *function* of the circuit**
    - According to *Truth Table (K-map, Karnaugh Map)*
  - The **related circuit can be deleted** to simplify the circuit
- **s-a-0 just be replaced by Line 0; s-a-1 by Line 1**
- **Undetectable faults = Redundant faults**





# Fault Detection

---

- ❑ **Why Logical Fault Modeling**
- ❑ **Fault Detection**
- ❑ **Sensitization**
- ❑ **Detectability**
  - **Detectable vs Undetectable**
- ❑ **Undetectable Faults**
- ❑ **Test Set**
- ❑ **Test Generation Flow**
- ❑ **Fault Equivalence**
  - **Equivalence Fault Collapsing**



# Test Set

---

- ❑ **Complete detection test set:** A set of tests/test inputs that detect any detectable faults in a class of faults
- ❑ **Test Quality:** The **quality** of a test set is measured by **test/fault coverage**
- ❑ **Fault coverage:** Fraction of faults that are detected by a test set
- ❑ The fault coverage can be determined by **fault simulation**
  - >95% is typically required for **single stuck-at fault** model
  - >99.9% in IBM
  - Four 9 principle: 99.99%



# Fault Detection


---

- ❑ **Why Logical Fault Modeling**
- ❑ **Fault Detection**
- ❑ **Sensitization**
- ❑ **Detectability**
  - **Detectable vs Undetectable**
- ❑ **Undetectable Faults**
- ❑ **Test Set**
- ❑ **Test Generation Flow**
- ❑ **Fault Equivalence**
  - **Equivalence Fault Collapsing**



# Typical Test Generation Flow

---

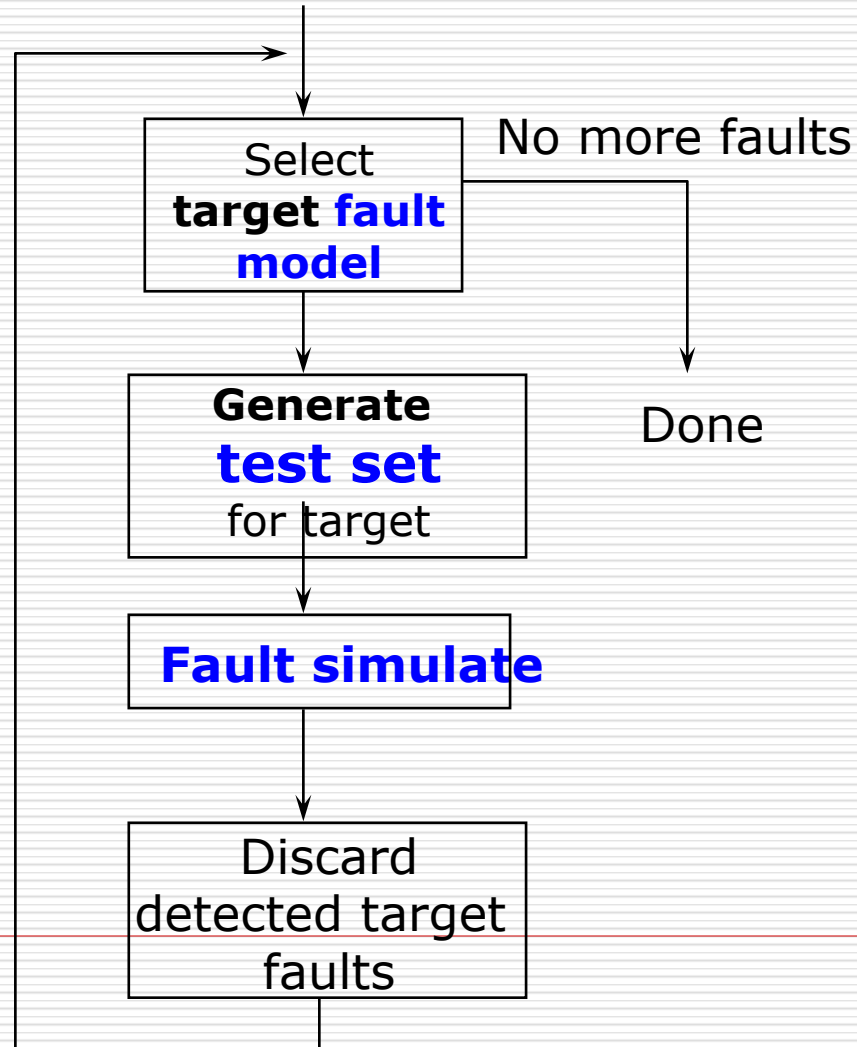

# Fault Detection

---

- ☐ **Why Logical Fault Modeling**
- ☐ **Fault Detection**
- ☐ **Sensitization**
- ☐ **Detectability**
  - **Detectable vs Undetectable**
- ☐ **Undetectable Faults**
- ☐ **Test Set**
- ☐ **Test Generation Flow**
- ☐ **Fault Equivalence**
  - **Equivalence Fault Collapsing**



# Fault Equivalence (1/3)

---

- A test  $t$  **distinguishes** between faults  $\alpha$  and  $\beta$  if  $\mathbf{z}_{\alpha}(t) \oplus \mathbf{z}_{\beta}(t) = 1$
- Two **faults**,  $\alpha$  &  $\beta$  are said to be **equivalent** in a circuit, iff the **function under**  $\alpha$  is equal to the **function under**  $\beta$  for any input combination (sequence) of the circuit.
  - $\mathbf{z}_{\alpha}(t) = \mathbf{z}_{\beta}(t)$  for all  $t$
  - **No test** can distinguish between  $\alpha$  and  $\beta$
  - Any test which detects one of them detects all of them







# Fault Equivalence (2/3)

---

- **AND** gate
  - All **s-a-0** faults are equivalent
- **OR** gate
  - All **s-a-1** faults are equivalent
- **NAND** gate
  - All the **input s-a-0** faults and the **output s-a-1** faults are equivalent
- **NOR** gate
  - All **input s-a-1** faults and the **output s-a-0** faults are equivalent
- **Inverter**
  - **Input s-a-1** and **output s-a-0** are equivalent
  - **Input s-a-0** and **output s-a-1** are equivalent
- Key concept: all **CV (Controlling Value)** are equivalent



# Fault Equivalence (3/3)

GATE Type	CV (Controlling Value)	NCV (Non-Controlling Value)
<b>AND</b>	<b>0</b> 	<b>1</b>
<b>NAND</b>	<b>0</b> 	<b>Only output inv 1</b>
<b>OR</b>	<b>1</b> 	<b>0</b>
<b>NOR</b>	<b>1</b> 	<b>Only output inv 0</b>
<b>INV</b>	<b>0 vs 1; 1 vs 0</b>	
<b>XOR XNOR</b>	<b>0 vs 1; 1 vs 0 0 vs 0; 1 vs 1</b>	<b>XOR=1 for different inputs XNOR=1 for Same inputs</b>





# Fault Detection

---





- ❑ **Why Logical Fault Modeling**
- ❑ **Fault Detection**
- ❑ **Sensitization**
- ❑ **Detectability**
  - **Detectable vs Undetectable**
- ❑ **Undetectable Faults**
- ❑ **Test Set**
- ❑ **Test Generation Flow**
- ❑ **Fault Equivalence**
  - **Equivalence Fault Collapsing**



# Equivalence Fault Collapsing (1/3)
    
## (N)AND vs (N)OR

- *n inputs, 1 output under SA0/SA1*  
 $\Rightarrow 2(n+1) = 2+2$
- **By Controlling Value:** only ONE from n-inputs & 1 output is enough  $\Rightarrow$  delete #n faults
  - **n+2** instead of **2n+2** faults need to be considered for n-input gates



# Equivalence Fault Collapsing (2/3)

## Wire

---




- Equivalence in a wire [between two endpoints]
  - Fault equivalence
    - **A sa0**  $\leftrightarrow$  **B sa0**
    - **A sa1**  $\leftrightarrow$  **B sa1**
  - No need to consider B sa0 and B sa1
  - Summary: Both ends of a wire are fault equivalence because same voltage value


 
# Equivalence Fault Collapsing (3/3)

- ❑ Two/Multiple **equivalent faults** are detected **by exactly the same tests**
  - The following three faults are equivalent
  - That is, **same FEs along propagation path**



---

*Thank You for  
Your Attention & Participation!*

